

ELEC 204

Digital Design Preliminary

Lab Report

Pre Lab: 04

Name: Burhan Karahasan

Date: 27.12.2020

LED PING-PONG GAME


Q5.1 In the given code, there are two processes; one for clock dividing and another one demanded purpose. The clock divider process is sensitive to clock change and it increases a counter at the rising edges. When counter reaches to a previously assigned value, it causes an alternation in the output signal. In this code the clock divider decreases the frequency from 50MHz to $\frac{1}{2}\text{Hz}$. The second process is sensitive to the alternating signal -

State Diagram

(P)

There are 4 LED outputs whose names are A, B, C and D respectively. I defined 6 different states called A_1, B_1, C_1, D_1, C_2 and B_2 . Names indicate which LED is on, for example, B LED gives high when the present state is either B_1 or B_2 .

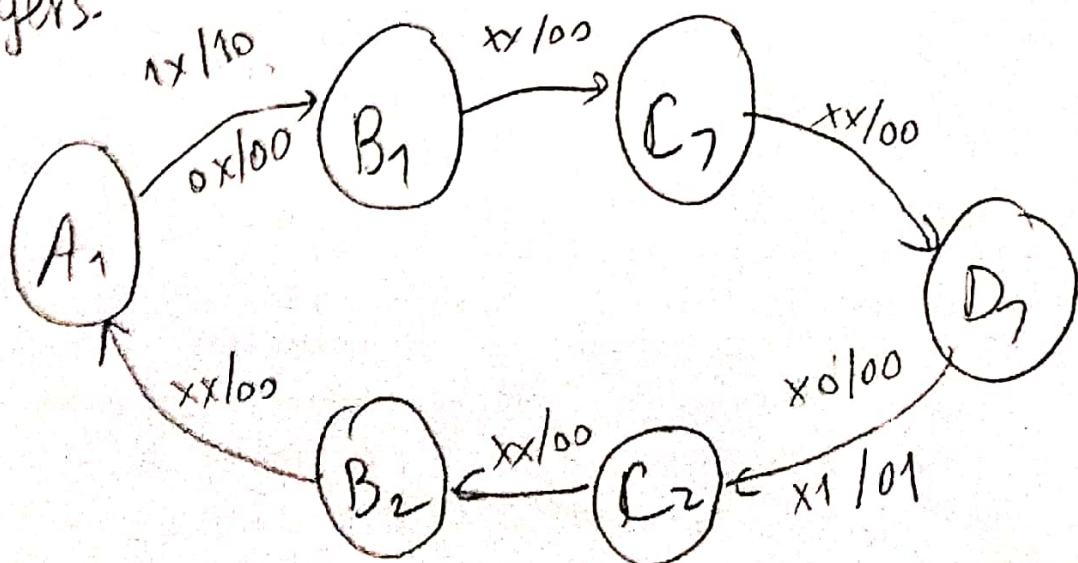I defined 2 inputs called Left and Right which are taking their values from two push buttons. I defined two more outputs namely X and Y which represent the score earned for players.



②

State Table

Present State	Next State	Output			
		LR =			
		00	01	10	11
A: 000001	000010	00	00	10	10
B ₁ : 000010	000100	00	00	00	00
		00	00	00	00
C ₁ : 000100	001000				
		00	01	00	01
D: 001000	010000				
		00	00	00	00
C ₂ : 010000	100000				
		00	00	00	00
B ₂ : 100000	000001				

L = Left Push
R = Right Push

X = catch for A
Y = catch for D

State Equations (D-type FF)

$$D_6 = Q_6^+ = Q_5$$

$$X = Q_1 L$$

$$D_5 = Q_5^+ = Q_4$$

$$Y = Q_4 R$$

$$D_4 = Q_4^+ = Q_3$$

$$A = Q_1$$

$$D_3 = Q_3^+ = Q_2$$

$$B = Q_2 + Q_6$$

$$D_2 = Q_2^+ = Q_1$$


$$C = Q_5 + Q_3$$

$$D_1 = Q_1^+ = Q_6$$

$$D = Q_4$$

Circuit Design 1

(3)

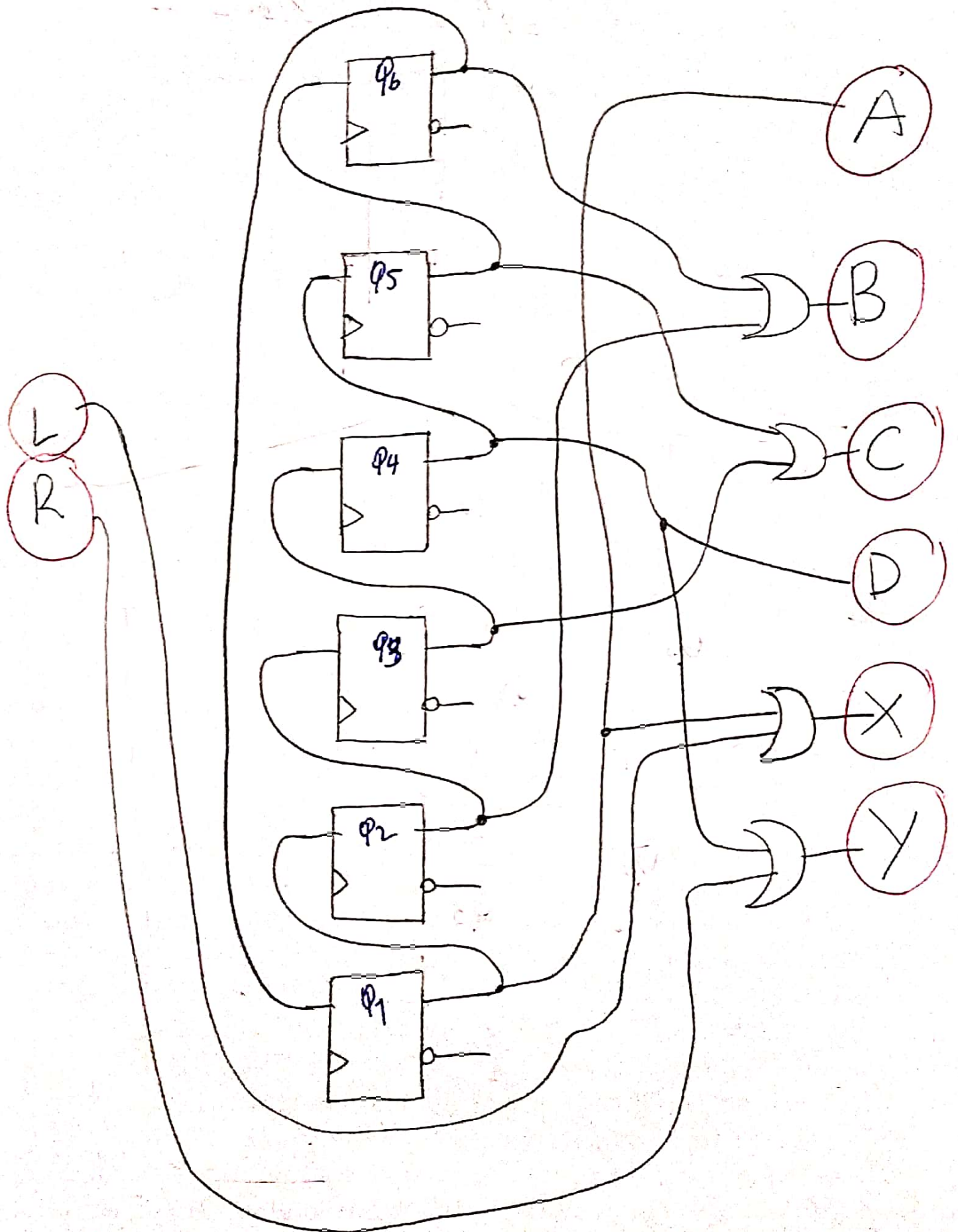

Score Counter

④

X and Y will be the inputs of score counter component.

The circuit I use is normally a clock divider circuit whose last output gives the clock in demanded period. However, if we take all of the outputs as a vector then it becomes a binary counter clock. For the score counting purpose we define the first input as X (or Y). It utilizes 4 D type FFs.

